

ELC 2137 Lab 10: 7-segment Display with Time-Division Multiplexing

Jake Simmons

April 14, 2020


Summary

The purpose of this lab was to learn how to use the technique called Time-Division Multiplexing. We are using Time-Division Multiplexing to slow down the signals going to the 4 digit display. This is so there will be enough time for a human to process and see what is actually being displayed. First, a counter module was made and successfully simulated. Secondly, the sseg4 from a previous lab was modified and the counter was added to the module. A schematic of the new, sseg4TDM, is provided. After testing sseg4TDM, the top level module, calclab10, was created. The top level module toplab9 was used in this module which was also created in a previous lab.

Q&A

- What are the three main “groups” of the RTL definition of sequential logic?
 - The three main groups of the RTL definitions of sequential logic is event driven, clock driven and pulse driven.
- Copy Figure 10.3b onto your own paper (or do it electronically) and draw three boxes around the components that belong to each group. Include your annotated figure in your report.

Figure 1: 10.3B Labeling

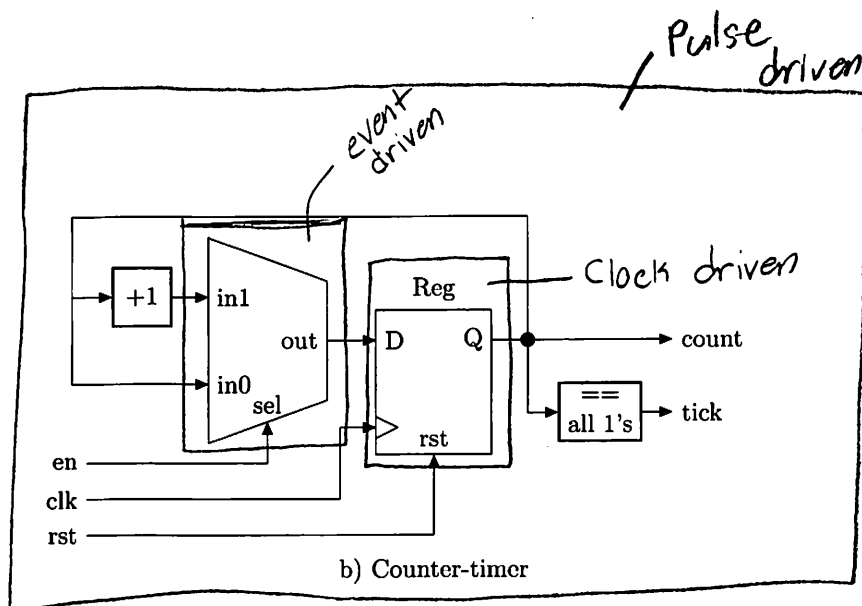

- If instead of a counter, you wanted to make a shift register that moved the input bits from right to left (low to high). What would you put on the line $Q_{next} = /*???*/$?
 - To make a shift register that moved bits from right to left, you would put on the line $Q_{next} = Q_{reg} - 1;$

Results

Time (ns):	0	20	40	60	80	100	120	140	160	180	200	220	240	260	280	300	320
clk	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
en	0	1	1	1	0	0	1	0	1	0	1	1	0	1	1	1	1
rst	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
count	X	1	2	3	4	5	6	7	8	9	a	b	c	d	e	f	0
tick	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0

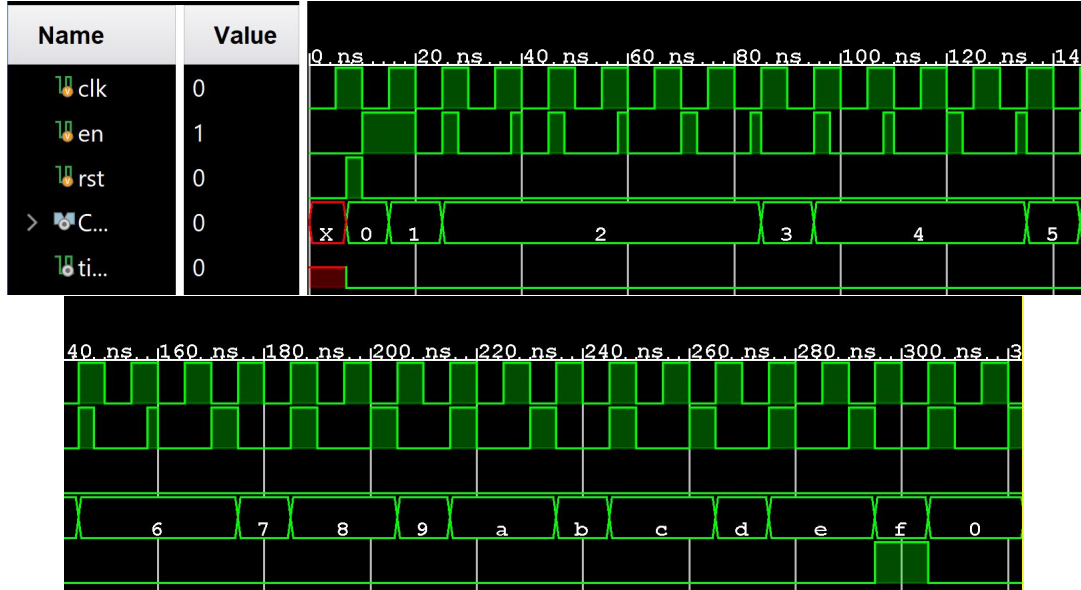


Figure 2: Counter simulation waveform and ERT

Time (ms):	0	2	4	6	8	10	12	14	16	18	20	22	24	26	28	30	32	34	36	38	40
clk	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
rst	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
data	0	1	1	2	3	4	4	5	6	7	8	8	9	a	b	c	c	d	e	e	f
hexdec	0	1	1	1	1	1	1	1	1	1	1	0	0	0	0	1	1	1	0	0	0
seg	40	79	79	24	40	40	40	40	40	40	3f	3f	30	08	40	79	79	40	40	40	40
dp	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
an	e	e	e	e	e	d	d	d	7	7	7	e	e	e	d	d	d	b	b	b	7


 


Figure 3: sseg4TDM simulation waveform and ERT

[illegible]

Figure 5: calclab10 Schematic

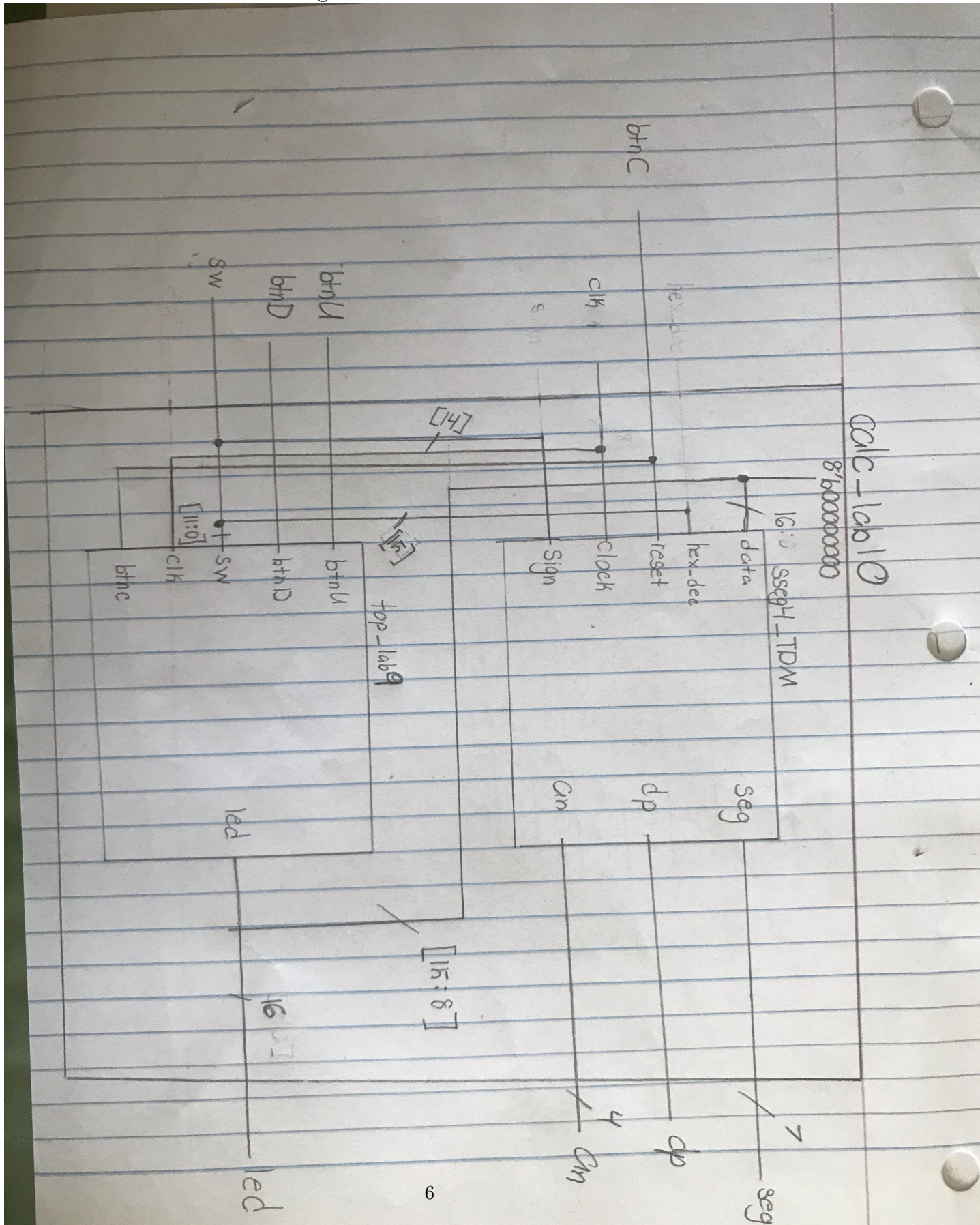

Code

Listing 1: Counter Module

```
'timescale 1ns / 1ps
// ELC 2137 Jake Simmons 2020-7-4

module Counter #(parameter N=1) (
    input clk, rst, en,
    output [N-1:0] count ,
    output tick
);
    // internal signals
    reg [N-1:0] Q_reg , Q_next;
    // register (state memory)
    always @(posedge clk, posedge rst)
        begin
            if (rst)
                Q_reg <= 0;
            else
                Q_reg <= Q_next;
        end
    // next -state logic
    always @*
        begin
            if (en)
                Q_next = Q_reg + 1;
            else
                Q_next = Q_reg; // no change
        end
    // output logic
    assign count = Q_reg;
    assign tick = (Q_reg=={N{1'b1}}) ? 1'b1 : 1'b0;
endmodule // counter
```

Listing 2: Counter Test Bench

```
'timescale 1ns / 1ps
//ELC 2137 Jake Simmons 2020-7-4

module counter_test();
    reg clk, en, rst;
    wire [3:0] count;
    wire tick;

    Counter #(N(4)) count1( .tick(tick), .clk(clk),
        .en(en), .rst(rst), .count(count) );

    // clock runs continuously

    always begin
```



```

        en = 0; #10;
        en = 1; #3;
        en = 1; #2;
        en = 0; #10;
        en = 1; #3;
        en = 1; #2;
        en = 0; #10;
        en = 1; #3;
        en = 1; #2;
        en = 0; #10;
        en = 1; #3;
        en = 1; #2;
        en = 0; #10;
        en = 1; #3;

    $finish;

end
endmodule

```

Listing 3: sseg4TDM Module

```

`timescale 1ns / 1ps
//ELC 2137 2020-4-7

module sseg4_TDM(
    input clock,
    input reset,
    input [15:0] data,
    input hex_dec,
    input sign,
    output [6:0] seg,
    output dp,
    output [3:0] an
);

    wire [1:0] digit_sel;
    wire [15:0] W1 ;
    wire [15:0] W2 ;
    wire [3:0] W3;
    wire [6:0] W4;
    wire [3:0] W5;
    wire W6;
    wire [1:0] W7;

    Counter #(.N(18)) timer( .clk(clock), .en(1'b1), .tick(W7), .rst(reset)
        );

    Counter #(.N(2)) counter2( .clk(clock),.en(W7),.count(digit_sel), .rst(
        reset) );

    BCD11_2 B1( .in11(data[10:0]), .out11(W1));

    mux2 #(.N(16)) B2( .in0(data), .in1(W1), .sel(hex_dec), .out(W2));

```

```

mux4 B3( .in0(W2[3:0]), .in1(W2[7:4]), .in2(W2[11:8]), .in3(W2[15:12]),
        .sel(digit_sel), .out(W3));

sseg_decoder B5( .num(W3), .sseg(W4));

mux2 #(.N(7)) B6( .in0(W4), .in1(7'b0111111), .out(seg) , .sel(W6));

and G2( W6, sign, ~W5[3]);

annode_decoder B7( .in(digit_sel), .out(W5));

assign dp = 1;
assign an = W5;
endmodule

```

Listing 4: sseg4TDM Test Bench

```

`timescale 1ns / 1ps
//ELC 2137 2020-7-4

module sseg4_TDM_test();
    reg clock;
    reg reset;
    reg [15:0] data;
    reg hex_dec;
    reg sign;
    wire [6:0] seg;
    wire dp;
    wire [3:0] an;

    sseg4_TDM sseg4( .clock(clock), .reset(reset), .data(data), .hex_dec(
        hex_dec),
        .sign(sign), .seg(seg), .dp(dp), .an(an));

    // clock runs continuously

    always begin

        clock = ~clock; #10;

    end

    // this block only runs once

    initial begin
        data = 0; hex_dec = 0; reset = 1; clock = 0; sign = 0; #2621440;
        data = 1; hex_dec = 1; reset = 0; sign = 0; #2621440;
        data = 2; hex_dec = 1; reset = 0; sign = 0; #2621440;
        data = 3; hex_dec = 1; reset = 0; sign = 0; #2621440;
        data = 4; hex_dec = 1; reset = 0; sign = 0; #2621440;
        data = 5; hex_dec = 1; reset = 0; sign = 0; #2621440;
    end

```

```

        data = 6; hex_dec = 1; reset = 0;  sign = 0;  #2621440;
        data = 7; hex_dec = 1; reset = 0;  sign = 0;  #2621440;
        data = 8; hex_dec = 0; reset = 0;  sign = 1;  #2621440;
        data = 9; hex_dec = 0; reset = 0;  sign = 1;  #2621440;
        data = 10; hex_dec = 0; reset = 0;  sign = 1;  #2621440;
        data = 11; hex_dec = 0; reset = 0;  sign = 1;  #2621440;
        data = 12; hex_dec = 1; reset = 0;  sign = 1;  #2621440;
        data = 13; hex_dec = 1; reset = 0;  sign = 1;  #2621440;
        data = 14; hex_dec = 0; reset = 0;  sign = 0;  #2621440;
        data = 15; hex_dec = 0; reset = 0;  sign = 0;  #2621440;

    $finish;

end
endmodule

```

Listing 5: calclab10 Module

```

`timescale 1ns / 1ps
//ELC 2137 Jake Simmons 2020-4-8

module calc_lab10(
    input clk,
    input btnU,
    input btnD,
    input [11:0] sw,
    input btnC,
    output [15:0] led,
    output [6:0] seg,
    output dp,
    output [3:0] an
);
    wire [7:0] W1;

    sseg4_TDM disp_unit( .data({8'b00000000, W1}), .hex_dec(sw[15]),
        .reset(btnC), .clock(clock), .sign(sw[14]),
        .seg(seg), .dp(dp), .an(an));

    top_lab9 calc_unit( .btnU(btnU), .btnD(btnD), .sw(sw[11:0]),
        .clk(clk), .btnC(btnC), .led(led) );

    assign w1 = led[15:8];
endmodule

```
