

# ELC 2137 Lab 2: Transistor Logic Gates

Jake Simmons and Haonan Jin

January 27, 2020

## Summary

The purpose of this lab was to build and explore the behaviors of logic gates. We first built an OR Gate, second a Not Gate and third a Nor Gate. The last logic gate was a combination of two Not Gates and a single Nor Gate.

## Q&A

1. What logic operation does the Final gate implement?
  - (a) The logic operation that the Final gate implements is an And Gate.

## Results

Table 1: Truth Table of the Final gate.

A	B	Led
0	0	0
0	1	0
1	0	0
1	1	1

## Circuit Demonstration Page

Student names: Jake Simmons Haonan Jin

### Instructor Initials

Pushbutton "Or Gate"

BH

Transistor Not gate

BH

Transistor Nor gate

BH


Transistor unknown gate

BH


### Diagrams

On each of the circuits below, draw the current paths and note whether each switch, transistor, and LED is ON or OFF.

Inverter:

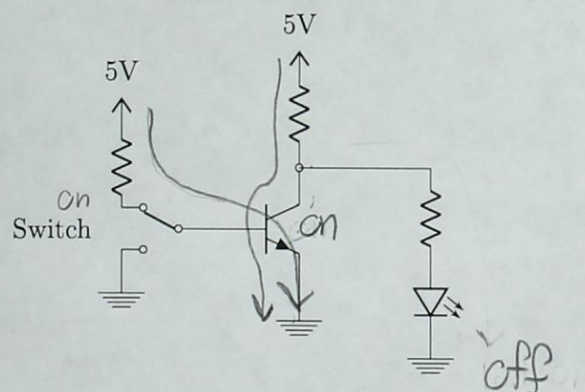

NOR:

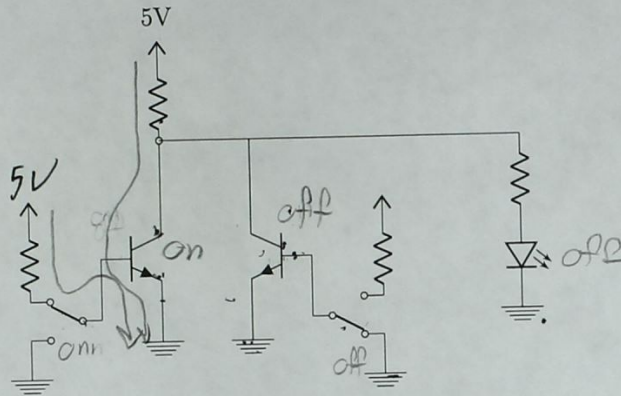

Final gate:

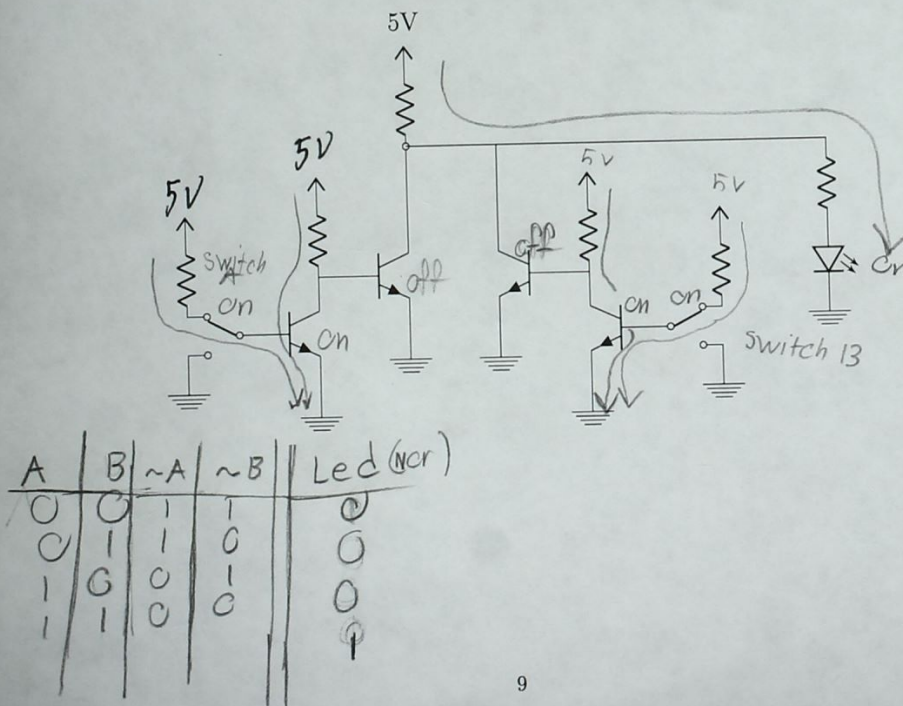


Figure 1: Schematics and drawing of current path for each logic gate

**Code**