ELC 2137 Lab 9: ALU

Jake Simmons

April 1, 2020

Summary

The purpose of this lab was to create an Arithmetic Logic Unit capable of operations. As well as explore the ideas of combinational and regular sequentional logic in SR Latches, D Latches, D flip-flop and D registers. In this lab, a Register module was created and successfully tested. An ALU module was created and successfully tested.

Q&A Results

Time (ns):	0-5	5-10	10-15	15-20	20-25	25-30	30-35	35-40	40-45	45-50	50-55
D (hex)	0	0	A	A	3	3	0	0	$0\rightarrow 6$	6	6
clk	0	1	0	1	0	1	0	1	0	1	0
en	0	0	1	1	$1 \rightarrow 0$	$0 \rightarrow 1$	$1\rightarrow0$	0	$0\rightarrow 1$	1	1
rst	0	$0\rightarrow 1$	0	0	0	0	0	0	0	0	0
Q (hex)	X	$X\rightarrow 0$	0	A	A	A	A	A	A	6	6



Figure 1: ERT and Simultion Waveforms of Register

Time (ns):	0-10	10-20	20-30	30-40	40-50	50-60
in0 (dec)	5	A	1	3	5	F
in1 (dec)	5	5	2	4	6	\mathbf{C}
op (dec)	0	1	2	3	4	5
out (dec)	A	5	0	7	3	F

Name	Value	0 ns	10 ns 15 ns	20 ns	30. ns	35 ns	40 ns 45 ns	50 ns
> Win0[7:0]	03	05	0a	01		03	05	0£
> ₩in1[7:0]	04	0	05	02		04	06	0c
> ₩op[7:0]	03	00	01	02		03	04	05
> W out[7:0]	07	0a	05	00		07	03	0£

Figure 2: ERT and Simulation Waveforms of ALU



Figure 3: Top Level Simulation Waveforms

Code

Listing 1: Register Module

```
'timescale 1ns / 1ps
//ELC 2137 Jake Simmons 2020-3-26
module register_2 #(parameter N=1)
   input clk, rst, en,
   input [N-1:0] D,
   output reg [N-1:0] Q
   always @(posedge clk, posedge rst)
      begin
         if (rst==1)
            Q <= 0'b0;
         else if (en==1)
            Q \le D;
   end
   // Notes: // - Reset is asynchronous , so this
  // block needs to execute when rst
   // goes high.
  // - We want enable to be synchronous
  // (i.e. only happens on rising
   // edge of clk), so it is left out
   // of "sensitivity" list.
endmodule
```

Listing 2: ALU Module

```
'timescale 1ns / 1ps
//ELC 2137 Jake Simmons 2020-3-29
module ALU#(parameter N=8)
   output reg[N-1:0] out,
   input [N-1:0] in0,
   input [N-1:0] in1,
   input [3:0] op
   );
   // Local parameters
   parameter ADD=0;
   parameter SUB=1;
   parameter AND=2;
  parameter OR=3;
   parameter XOR=4;
   always @*
      begin
         case(op)
            ADD: out = in0 + in1;
            SUB: out = in0 - in1;
            AND: out = in0 & in1;
            OR: out = in0 | in1;
```

```
XOR: out = in0 ^ in1;
    default: out = in0;
    endcase
    end
endmodule
```

Listing 3: Lab 9 Top Module

```
'timescale 1ns / 1ps
//ELC 2137 Jake Simmons 2020-3-30
module top_lab9(
   input btnU,
   input btnD,
   input [11:0] sw,
   input clk,
   input btnC,
   output [15:0] led
   );
   wire [7:0] W1;
   wire [7:0] W2;
   register_2 #(.N(8)) r1( .D(sw[7:0]), .en(btnD), .clk(clk), .Q(W1), .rst
      (btnC)
   );
   ALU alu( .in1(W1), .in0(sw[7:0]), .op(sw[11:8]), .out(W2)
   register_2 #(.N(8)) r2( .D(W2), .en(btnU), .clk(clk), .rst(btnC), .Q(
      led[15:8])
   );
   assign led [7:0] = W1;
endmodule
```

Listing 4: Register Test Bench Code

```
'timescale 1ns / 1ps
//ELC 2137 Jake Simmons 2020-3-26

module register_2_test();

   reg [3:0] D;
   reg clk, en, rst;
   wire [3:0] Q;
   register_2 #(.N(4)) r(.D(D), .clk(clk),
    .en(en), .rst(rst), .Q(Q) );

// clock runs continuously
   always begin
      clk = ~clk; #5;
   end
```

```
// this block only runs once
initial begin
    clk = 0; en = 0; rst = 0; D = 4'h0; #7;
    rst = 1; #3; // reset
    D = 4'hA; en = 1; rst = 0; #10;
    D = 4'h3; #2;
    en = 0; #5;
    en = 1; #3;
    D = 4'h0; #2;
    en = 0; #10;
    en = 1; #2;
    D = 4'h6; #11;
    $finish;
end
endmodule
```

Listing 5: ALU Test Bench Code

```
'timescale 1ns / 1ps
//ELC 2137 Jake Simmons 2020-3-29
module ALU_Test();
  reg [7:0] in0;
  reg [7:0] in1;
  reg [7:0] op;
   wire [7:0] out;
   ALU alu(
   .in0(in0), .in1(in1), .op(op), .out(out)
  );
   initial
      begin
         in0 = 8'd5; in1 = 8'd5; op = 0; #10;
         in0 = 8'd10; in1 = 8'd5; op = 1; #10;
         in0 = 8'd1; in1 = 8'd2; op = 2; #10;
         in0 = 8'd3; in1 = 8'd4; op = 3; #10;
         in0 = 8'd5; in1 = 8'd6; op = 4; #10;
         in0 = 8'd15; in1 = 8'd12; op = 5; #10;
      end
endmodule
```