

ELC 2137 Lab 9: ALU

Jake Simmons

March 31, 2020

Summary

The purpose of this lab was to create an Arithmetic Logic Unit capable of operations. As well as explore the ideas of combinational and regular sequential logic in SR Latches, D Latches, D flip-flop and D registers. In this lab, a Register module was created and successfully tested. An ALU module was created and successfully tested.

Q&A

Results

Time (ns):	0-5	5-10	10-15	15-20	20-25	25-30	30-35	35-40	40-45	45-50	50-55
D (hex)	0	0	A	A	3	3	0	0	0→6	6	6
clk	0	1	0	1	0	1	0	1	0	1	0
en	0	0	1	1	1→0	0→1	1→0	0	0→1	1	1
rst	0	0→1	0	0	0	0	0	0	0	0	0
Q (hex)	X	X→0	0	A	A	A	A	A	A	6	6

 


Figure 1: ERT and Simulation Waveforms of Register

Name	Value
in0[7:0]	03
in1[7:0]	04
op1[7:0]	03
out[7:0]	07

Name	Value
btnU	1
btnD	0
clk	1
btnC	0
sw[11:0]	07a
led[15:0]	8e14

The timing diagram displays the following signals over a 95 ns period:

- btnU**: A constant high signal (1).
- btnD**: A constant low signal (0).
- clk**: A constant high signal (1).
- btnC**: A constant low signal (0).
- sw[11:0]**: A 12-bit bus signal that transitions from 0000 to 07a at approximately 55 ns.
- led[15:0]**: A 16-bit bus signal that transitions from 0000 to 8e14 at approximately 55 ns.

2

Code

Listing 1: Register Module

```
'timescale 1ns / 1ps
//ELC 2137 Jake Simmons 2020-3-26

module register_2 #(parameter N=1)
(
    input clk, rst, en,
    input [N-1:0] D,
    output reg [N-1:0] Q
);
always @(posedge clk, posedge rst)
    begin
        if (rst==1)
            Q <= 0'b0 ;
        else if (en==1)
            Q <= D ;
    end
    // Notes: // - Reset is asynchronous , so this
    // block needs to execute when rst
    // goes high.
    // - We want enable to be synchronous
    // (i.e. only happens on rising
    // edge of clk), so it is left out
    // of "sensitivity" list.
endmodule
```

Listing 2: ALU Module

```
'timescale 1ns / 1ps
//ELC 2137 Jake Simmons 2020-3-29

module ALU#(parameter N=8)
(
    output reg[N-1:0] out,
    input [N-1:0] in0,
    input [N-1:0] in1,
    input [3:0] op
);
    // Local parameters
    parameter ADD=0;
    parameter SUB=1;
    parameter AND=2;
    parameter OR=3;
    parameter XOR=4;

    always @*
        begin
            case(op)
                ADD: out = in0 + in1;
                SUB: out = in0 - in1;
                AND: out = in0 & in1;
                OR:  out = in0 | in1;
```

```

        XOR: out = in0 ^ in1;
        default: out = in0;
    endcase
end
endmodule

```

Listing 3: Lab 9 Top Module

```

`timescale 1ns / 1ps
//ELC 2137 Jake Simmons 2020-3-30

module top_lab9(
    input btnU,
    input btnD,
    input [11:0] sw,
    input clk,
    input btnC,
    output [15:0] led
);
    wire [7:0] W1;
    wire [7:0] W2;

    register_2 #(.N(8)) r1( .D(sw[7:0]), .en(btnD), .clk(clk), .Q(W1), .rst
        (btnC)
    );

    ALU alu( .in1(W1), .in0(sw[7:0]), .op(sw[11:8]), .out(W2)
    );

    register_2 #(.N(8)) r2( .D(W2), .en(btnU), .clk(clk), .rst(btnC), .Q(
        led[15:8]
    );

    assign led [7:0] = W1;
endmodule

```

Listing 4: Register Test Bench Code

```

`timescale 1ns / 1ps
//ELC 2137 Jake Simmons 2020-3-26

module register_2_test();

    reg [3:0] D;
    reg clk, en, rst;
    wire [3:0] Q;
    register_2 #(.N(4)) r(.D(D), .clk(clk),
        .en(en), .rst(rst), .Q(Q) );

    // clock runs continuously
    always begin
        clk = ~clk; #5;
    end

```

```

// this block only runs once
initial begin
    clk = 0; en = 0; rst = 0; D = 4'h0; #7;
    rst = 1; #3; // reset
    D = 4'hA; en = 1; rst = 0; #10;
    D = 4'h3; #2;
    en = 0; #5;
    en = 1; #3;
    D = 4'h0; #2;
    en = 0; #10;
    en = 1; #2;
    D = 4'h6; #11;
    $finish;
end
endmodule

```

Listing 5: ALU Test Bench Code

```

`timescale 1ns / 1ps
//ELC 2137 Jake Simmons 2020-3-29

module ALU_Test();
    reg [7:0] in0;
    reg [7:0] in1;
    reg [7:0] op;
    wire [7:0] out;

    ALU alu(
        .in0(in0), .in1(in1), .op(op), .out(out)
    );
    initial
        begin
            in0 = 8'd5; in1 = 8'd5; op = 0; #10;
            in0 = 8'd10; in1 = 8'd5; op = 1; #10;
            in0 = 8'd1; in1 = 8'd2; op = 2; #10;
            in0 = 8'd3; in1 = 8'd4; op = 3; #10;
            in0 = 8'd5; in1 = 8'd6; op = 4; #10;
            in0 = 8'd15; in1 = 8'd12; op = 5; #10;
        end
endmodule

```
