

# ELC 2137 Lab 4: Subtractor

Jake Simmons and Haonan Jin

February 8, 2020

## Summary

In this experiment we made a subtractor from an adder. First we made an adder by combining two full adders which is a two-bit adder. Then we added three XOR Gates, this was because we needed to invert two of our inputs to generate the 2's complement. The third XOR Gate inverted the carry out bit because Figure 3 shows that the carry out bit in our expected results was the opposite of what mathematically it should have been.

## Q&A

1. Why did we use two full adders instead of a half adder and a full adder?
  - (a)
1. How many input combinations would it take to exhaustively test the adder/subtractor?
  - (a)
1. Why were the combinations given in the truth table chosen?
  - (a)
1. Do the results from your adder/subtractor match what you would expect from theory? Explain any discrepancies.
  - (a)

## Results

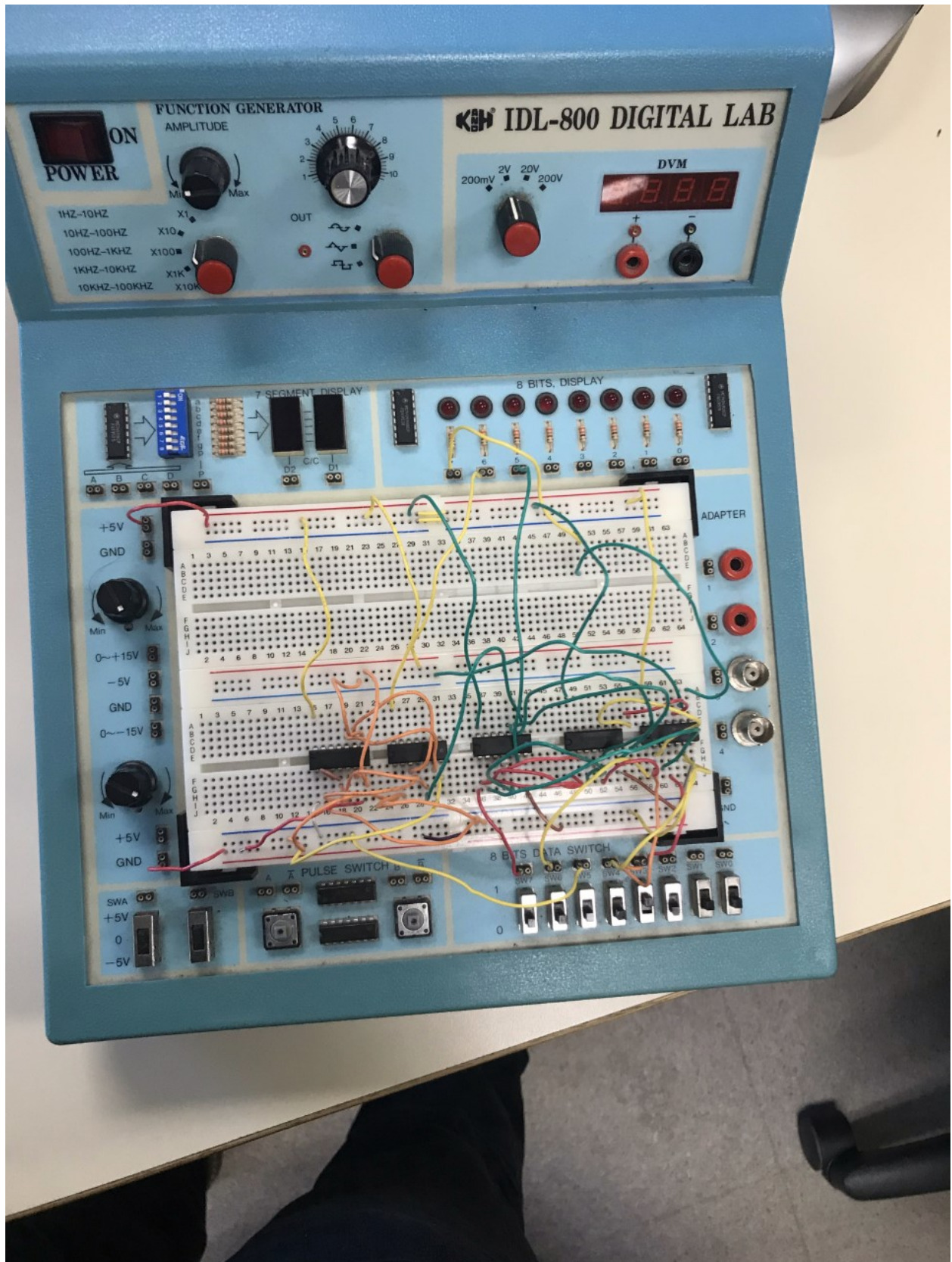


Figure 1: Picture of Assembled Circuit

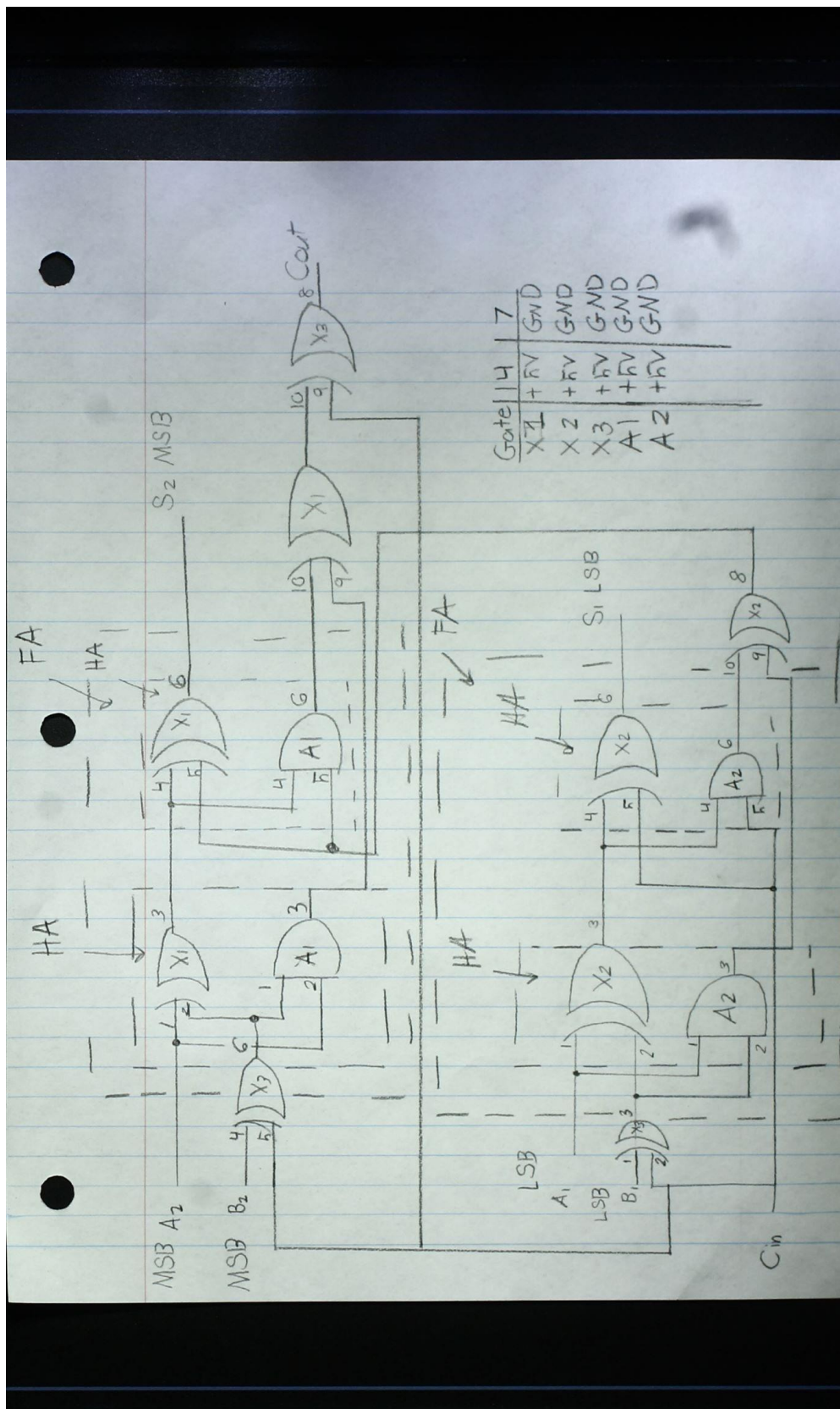


Figure 2: Two-Bit Adder/Subtractor Schematic



## Circuit Demonstration Page

Student names: Jake Simmons  
Haonan Jin

### Instructor Signatures

Separate Full Adders Del Walton

Two-Bit Adder Del Walton

Adder/Subtractor Del Walton

Inputs		Expected Results			Actual Results
A	B	B 2's comp	Sub	Dec	Sub
00	01	11	011	3	111
00	10	10	010	2	110
00	11	01	001	1	101
01	01	11	100	-4	000
10	01	11	101	-3	001
10	00	00	110	-2	010

Figure 3: Circuit Demonstration Page

**Code**