

Figure 10.2: 4-digit 7-seg driver (sseg4) schematic repeated from Lab 8

 


Figure 10.3: RTL schematics for a basic counter and our counter-timer